

## NEGATIVE IMPEDANCE REPEATERS

### DESIGN OF CIRCUITS USING SERIES TYPE

CONTENTS	PAGE
1. GENERAL . . . . .	1
2. CIRCUIT DESIGN FACTORS . . . . .	2
A. Required Gain . . . . .	2
B. Repeater Location . . . . .	2
C. Maximum Usable Gain . . . . .	2
D. Basis for Redesign . . . . .	3
E. Consideration of Loading End Sections . . . . .	3
F. Crosstalk Considerations . . . . .	8
G. Other Factors . . . . .	8
3. REPEATERS IN SERIES . . . . .	9
A. General . . . . .	9
B. Intermediate Repeaters . . . . .	9
C. Terminal Repeaters on the Same Circuit . . . . .	9
D. Terminal Repeaters on Switched Circuits . . . . .	9
4. SPECIAL SERVICE LINE CONSIDERATIONS . . . . .	10
A. General . . . . .	10
B. Intermediate Signaling Equipment . . . . .	10
C. Bridged Taps . . . . .	11
D. AC Operation of Repeaters . . . . .	11

#### 1. GENERAL

**1.01** This section discusses the considerations involved in the use of series-type negative impedance repeaters (E1 and E2 types) on exchange area trunks and special services lines. The more general engineering considerations involved in the use of these repeaters, such as return loss computations and other transmission data, are covered in other sections of this series. The use of these series elements in combination with shunt elements in L and T configurations is covered in other sections.

**1.02** This section is reissued to clarify maximum usable gains as related to crosstalk considerations, to change the maximum obtainable gain of a terminal repeater used with a nonloaded cable facility, and to update references to other BSP sections. The principal changes are denoted by change arrows.↯

**1.03** As with other repeaters, the use of these negative impedance series elements requires that suitable practices be followed to secure desired gains and, at the same time, to limit the likelihood of objectionable reactions due to instability, echo, overloading, or crosstalk.

**1.04** To simplify the design work, curves are included which indicate the maximum gains that ↯could be obtained based on the expected range of return losses on either side of the repeater. It should be noted, however, that usable maximum gains in circuits may be less than those based on return losses because of crosstalk considerations (see Part 2F). The maximum gain↯ curves are based on the assumption that the return losses at the critical frequency on both sides of the repeater may combine in phase. Since this will not occur in all cases, there may be some margin in specific cases, but this can not readily be determined in advance. Allowance is also made in the curves for departure of the network and other components

#### NOTICE

Not for use or disclosure outside the  
Bell System except under written agreement

from their optimum values, as well as for tube aging and power supply variations. This allowance, expressed as a return loss, is about 26 dB and is assumed to combine in phase (on a current basis) with other return losses on each side of the repeater. This is equivalent to about 10-percent reduction in impedance. It would, therefore, be possible, by measurements and special adjustments on a specific repeater, to obtain gains in the order of 0.5-dB greater than indicated by the curves. However, this is not an advisable procedure since tube replacements, aging, or other subsequent changes may reintroduce the variation and cause instability.

**1.05** The series element affords a transmission gain by introducing a negative impedance into the line. The magnitude of this negative impedance is adjustable by strappings on the repeater network. The gain is, therefore, an insertion gain which is equal in the two directions and its magnitude is determined by the network strappings and the line impedances in the two directions. Since these impedances may be different for the idle and talking conditions, the nominal gain is defined as the insertion gain produced between characteristic impedances. These gains are, therefore, approximately the same as those which exist under talking conditions though there will be some variations, particularly where a circuit with a terminal repeater is switched at that terminal to facilities with a variety of impedances.

**1.06** In the event that there are nonloaded facilities on one or both sides of the repeater, the gains noted on the curves in this section also contain an allowance for the improvement in transmission frequency characteristics and are, therefore, of the nature of effective gains. These are from 1- to 2-dB higher than the average single-frequency gain near 1000 Hz.

**1.07** Gains up to a maximum of about  $\pm 6$  dB are obtainable under the limitations of return losses and other factors. The gains can usually be estimated as discussed in this section and the network strappings can be prescribed.

**1.08** As outlined below, the proper strappings can in most cases be obtained from the strapping chart (Section 332-200-106.) Strappings for combinations of facilities not shown in that section may be determined by methods outlined in Section 852-305-103.

## 2. CIRCUIT DESIGN FACTORS

### A. Required Gain

**2.01** The gain required in a particular circuit is determined by the transmission objectives and other general engineering considerations. This gain required is one of the design factors which will determine the type of repeater to be used. Gain, as computed in this section, is the maximum obtainable gain with the series-type repeater under given circuit conditions.

### B. Repeater Location

**2.02** In the selection of a series repeater location, consideration should be given to the following:

- (a) The most favorable location on loaded facilities with 6 or more loading coils is near the middle of the circuit (not less than 3 coils on either side of the repeater). For shorter lines a terminal location is preferable because it results in a more uniform gain-frequency characteristic even though slightly higher gains might be obtained at a midpoint location. For nonloaded circuits, the preferable location for a single repeater is at the midpoint, regardless of the loss.
- (b) For a circuit made up of two sections of unlike facilities, a location at the junction will be preferable. This is particularly desirable for junctions between nonloaded and loaded facilities.
- (c) For a line made up of sections of more than two unlike facilities, the preferable location will be at a junction which gives the more favorable line return losses. The calculation of return losses is discussed in Section 852-305-100.

### C. Maximum Usable Gain

**2.03** The maximum usable repeater gain from the standpoint of singing is determined from the return losses of the fixed line sections on both sides of the repeater as outlined below.

#### 2.04 *Intermediate Repeaters:*

- (a) ***Loaded Facilities on Both Sides—Similar Impedances:*** Fig. 1 gives the maximum

usable gains as a function of the return losses of the two fixed lines.

(b) **Loaded Facilities on Both Sides—Dissimilar Impedances:**

When loaded facilities with unlike impedances are involved, corrections read from Fig. 2, based on the difference between the two return losses and the ratio of line impedances, both of which are added algebraically to the gain determined from Fig. 1 to give the maximum insertion gain obtainable. The 1000-Hz half-section characteristic impedances may be used in determining the impedance ratio. For purposes of network selection, the nominal gain should be determined in accordance with Section 852-305-103. As an example, let the line east have a return loss of 14 dB and the line west have a return loss of 8 dB. Assume an impedance ratio for east to west of 0.6. Figure 1 indicates an obtainable gain of 6.0 dB. Add to this a correction of -0.4 dB from Fig. 2 to obtain the maximum obtainable insertion gain of 5.6 dB. The actual network strapping to obtain this gain may be determined from the strapping charts in Section 332-200-106. The network should be selected for the lower cutoff facility. This facility is the Z1 of Fig. 2 of Section 852-305-103. Using this chart for the example above, the 5.6-dB insertion gain will be obtained by the 4.0-dB strapping if the west facility network is used ( $Z2/Z1 = 0.6$ ) or by the 8.5-dB strapping if the east facility network is used ( $Z2/Z1 = 1.66$ ).

(c) **Nonloaded Facilities on Both Sides:** As in the case of loaded facilities, Fig. 1 may be used to determine gain as discussed in Section 852-305-103.

(d) **Loaded Facilities on One Side, Nonloaded on the Other:** Gains are given in Fig. 3A and 3B.

**2.05 Terminal Repeaters:** For all types of facilities, use Fig. 1 (as discussed in Section 852-305-103) and assume 0-dB return loss on the switched side. Where more gain is required than this would indicate and in applications where repeating coils may be used at the circuit terminal, consideration should be given to the matched impedance method discussed in the 852-305-ZZZ sections.

**D. Basis for Redesign**


**2.06** If the obtainable gain is not high enough to meet design requirements, changes in the circuit layout may be considered, such as the following:

- (a) Selection of another repeater location
- (b) Installation of additional loading
- (c) Improvement of return loss, such as the correction of loading irregularities
- (d) Use of facilities with higher structural return loss
- (e) Assignment to facilities with lower loss.

**E. Consideration of Loading End Sections**

**2.07** In general, the repeater network can be adjusted to give the gains indicated in Fig. 1, 3A, or 3B. When loaded facilities are involved on one or both sides of the repeater, the end sections adjacent to the repeater should be determined within 5 percent of a loading section. There are three conditions of these end sections which are of concern in applications of E1 and E2 repeaters. These conditions determine whether the strapping of the repeater network can be determined entirely from the charts, whether field adjustment will be required, and whether building-out procedures will be needed. The conditions, summarized in Table A, are as follows:

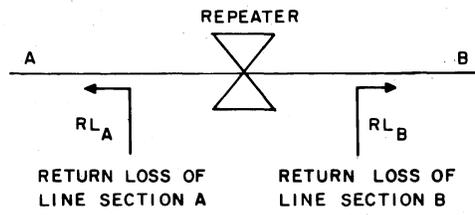- (a) When the end sections are within the ranges for which predetermined network strappings can be used to secure the gains indicated in Fig. 1, 3A, and 3B.
- (b) When the end sections are outside of the ranges covered by the predetermined network strappings but are still within ranges for which the gains indicated in Fig. 1, 3A, and 3B can be realized by gain tests and network strapping selection on the job.
- (c) When the end sections are so short that it would generally be impossible to obtain the gains indicated in Fig. 1, 3A, and 3B even with tests on the job.



NOTE: GAINS ARE BASED ON THE RETURN LOSS OF THE TWO LINE SECTIONS CONNECTED TO THE REPEATER.  
 WHEN THE CHARACTERISTIC IMPEDANCE OF LINE SECTION A DOES NOT EQUAL THAT OF LINE SECTION B, A GAIN CORRECTION, SHOWN ON FIG. 2, MUST BE ADDED.


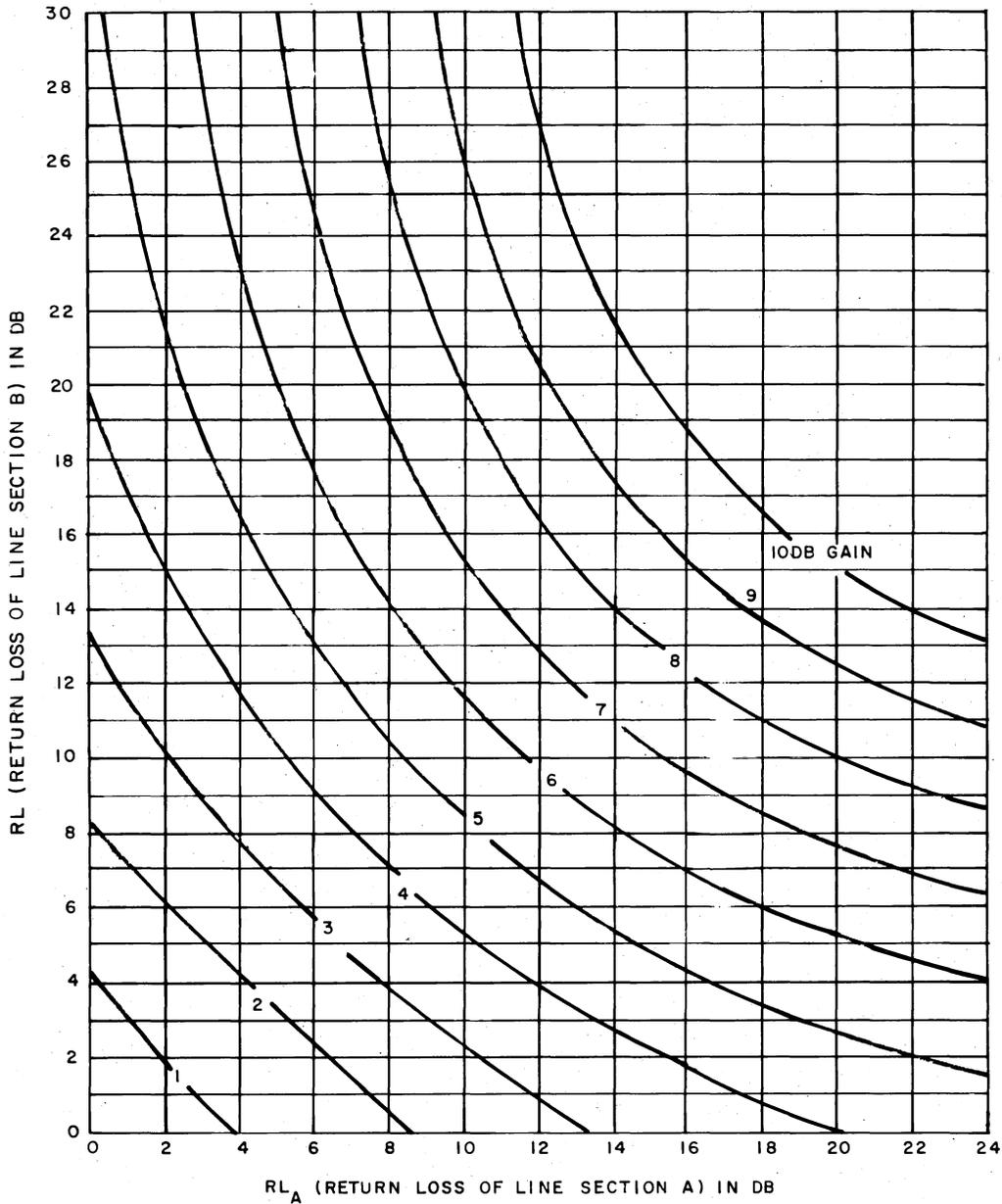


Fig. 1—Maximum Nominal Repeater Gain

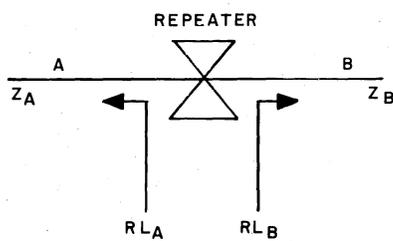

NOTE:  
 A AND B DESIGNATIONS  
 ARE SELECTED FOR  
 THE TWO LINE  
 SECTIONS SO THAT  
 $R_{L_A} > R_{L_B}$

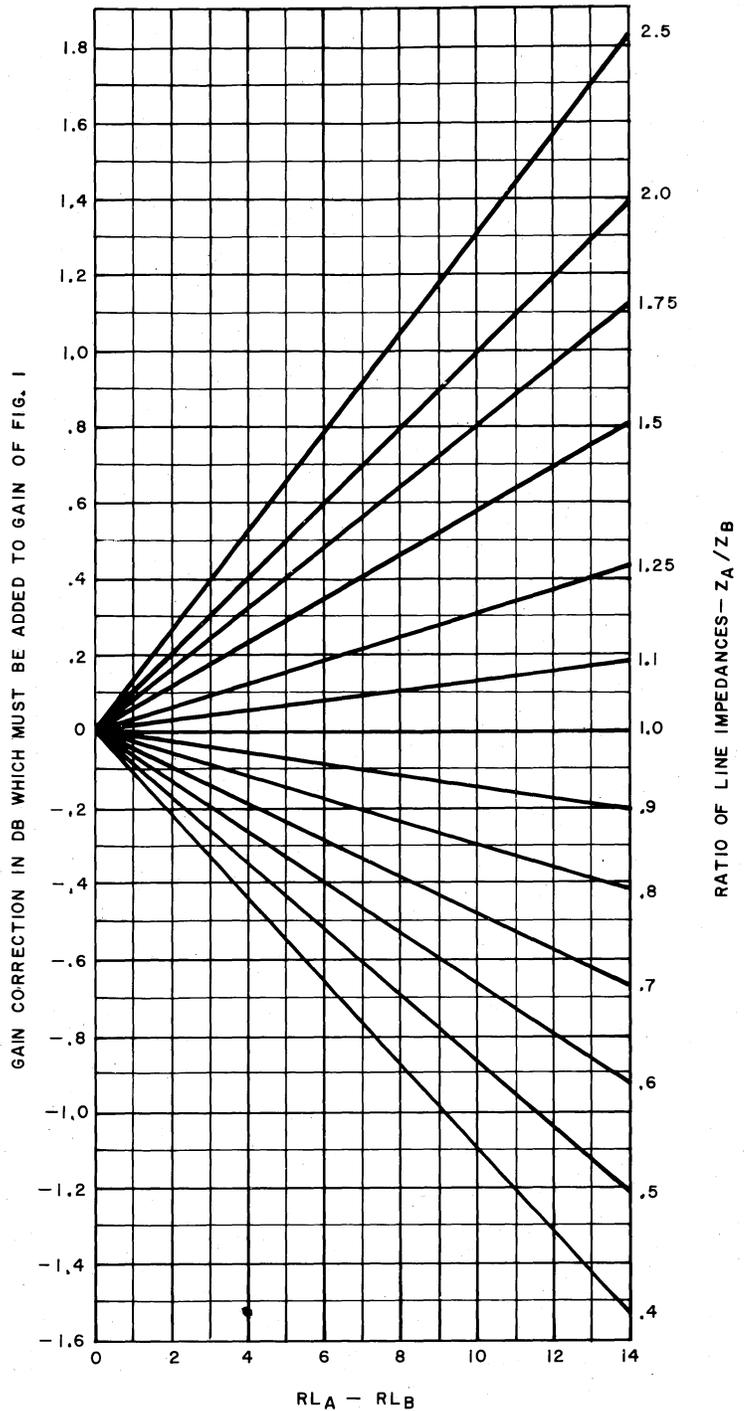


Fig. 2—Gain Correction for Unlike Line Impedances

2.08 Since building-out capacitors are now available both in the repeater and in inexpensive form for external use, it will in most cases be preferable to build out the end sections to be within the limits of (a) above rather than to require gain tests and network selection in the field. When building

out is used, the end sections should be adjusted to from 0.4 to 0.6 section whenever possible.

2.09 When building-out capacitors are used, the effect of the additional capacitance on the line loss should be considered. In determining this

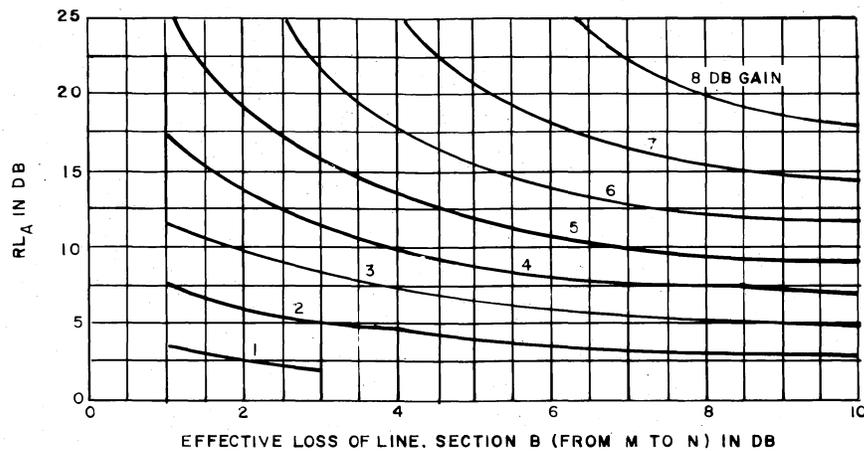
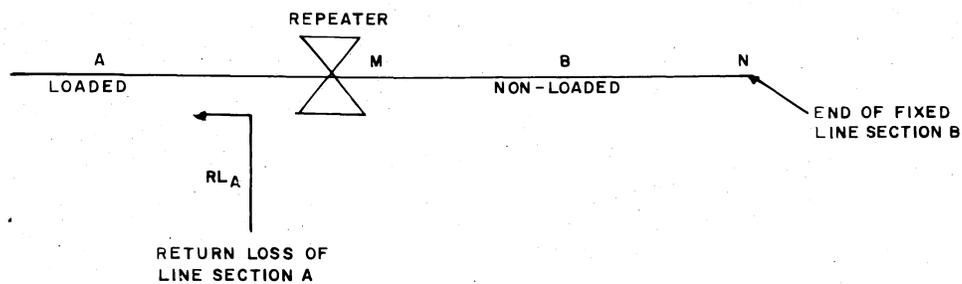


FIG. 3A  
END SECTION 0.3 TO 0.9

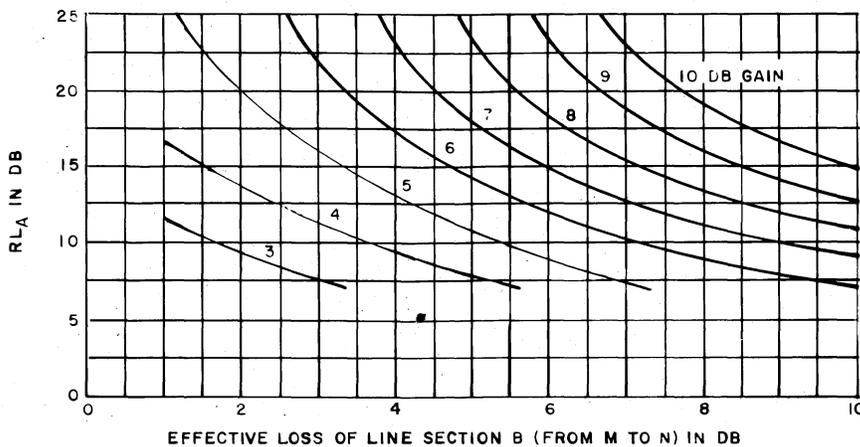


FIG. 3B  
END SECTION 0.9 TO 1.5

Fig. 3—Maximum Gain for Repeater Between Loaded and Nonloaded Lines

TABLE A

## END SECTION TREATMENT

END SECTIONS FOR WHICH GAINS INDICATED IN FIG. 1, 3A, or 3B . . . .

LINE CONDITIONS	CAN BE OBTAINED BY PREDETERMINED NETWORK STRAPPINGS	CAN BE OBTAINED BY NETWORK ADJUSTMENT ON JOB	CANNOT USUALLY BE OBTAINED
1. Terminal Repeaters			
a. Low cutoff facilities	0.4 to 1.25; 1.25 to 1.5 when return loss is 7 dB or more	0.3 to 0.4; 1.25 to 1.5 when return loss is less than 7 dB; 1.5 or more	0 to 0.3
b. High cutoff facilities	0.3 to 1.25; 1.25 to 1.5 when return loss is 7 dB or more	1.25 to 1.5 when return loss is less than 7 dB; 1.5 or more	0 to 0.3
2. Intermediate Repeaters			
a. Similar loading systems on both sides of repeater	0.3 to 0.5 for both; 0.4 to 1.25 for both	0.3 to 0.5 for one, over 0.5 for other; 0.4 to 1.25 for one, over 1.25 for other	0 to 0.3
b. Repeater between dissimilar loading systems	0.4 to 1.25 for both	0.4 to 1.25 for one, over 1.25 for other	0 to 0.4
c. Loaded facility on one side, nonloaded on other	0.3 to 0.9, Fig. 3A; 0.9 to 1.5, Fig. 3B	1.5 to 2	0 to 0.3

*Note:* If building-out capacitors are used, the preferable end sections after correction

*For cases 1a, 1b, 2b:* 0.4 to 0.6 section.

*For case 2a:* 0.4 to 0.5 section.

*For case 2c:* An end section of 0.3 section is generally desirable but, as indicated by Figs. 3A and 3B, higher gains may be possible for certain facilities with end sections of 0.9 to 1.5 section.

## SECTION 852-305-102

effect, consider the total build-out length between the adjacent loading points on the two sides of the repeater to be a loading section. Where the added building-out capacitance tends to correct a short section, no transmission penalty should be added. Where the building-out capacitance results in a longer than average section, a penalty should be added appropriate to the irregularity created.

### F. Crosstalk Considerations

#### Trunks

**2.10** The repeater location at which crosstalk is most severe is at the end of a trunk where connection is made to subscriber loops (ie, local office end of tandem and toll connecting trunks, or either end of direct interlocal trunks). If the gains of such terminal repeaters are kept within the values shown in the table below for various types of facilities, a crosstalk index of "GOOD" should be realized. (A more complete discussion of crosstalk index is contained in Sections 852-100-102 and 852-100-103.) These gain values are based on typical rms couplings for the various types of trunk facilities. In the case of nonstaggered twist cable, the coupling distribution is such that "POOR" crosstalk conditions may result even with small gains.

TYPE OF TRUNK FACILITY	MAXIMUM GAIN OF TERMINAL REPEATER
◆NL◆	◆6 dB◆
H88	6 dB
D88	5 dB
H135	5 dB
B135	3 dB
H175	3 dB

For intermediate repeaters the above gains may be increased by the amount of the trunk loss between the repeater location and the circuit terminal at the subscriber end. It should be noted, however, that in the above table for both terminal repeaters and intermediate repeaters, gains permitted by crosstalk may in certain cases exceed the maximum working gains from other design standpoints.

### Special Service Lines

**2.11** The gain values given in the table in 2.10 assume a distribution of subscriber loops for which the 1000-Hz loss of the average line is 4 dB. In the assignment of repeater gains on special service lines, the values in the above table may be decreased or increased accordingly as the 1000-Hz loss to the station terminal is less or greater than 4 dB, with a resultant index of "GOOD."

**2.12** If it is known that in a given splicing group or color group in a trunk cable, only a small fraction of the lines (less than 10 percent) are to be represented, the gains given above may be as much as doubled and an index of "GOOD" still be obtainable.

**2.13** The use of equalized 500-type sets properly zoned in subscriber loops should not affect the crosstalk index for repeatered trunks leaving that area, since the set gain is achieved only on longer loops, where crosstalk conditions are in general better than the index. However, on special service lines on which unequalized 500-type sets are used, the crosstalk susceptibility will be further increased by the 5-dB additional receiving gain of the 500-type set, and a crosstalk index of "GOOD" will not be achieved using the gains determined in 2.11. This principle applies, of course, to any other station equipment with higher receiving efficiency than the F1A-HA1 instrument.

### G. Other Factors

#### Repeater Overloading

**2.14** The E1 or E2 series repeater will handle output levels up to +14 dBm before significant gain compression takes place. For this reason these repeaters may be placed at any location on a line and operated at any gain permitted by other design limitations without danger of overloading.

#### Effect on Signaling Range

**2.15** The series repeater is coupled into a circuit by means of two separate transformer windings and introduces a loop dc resistance of about 40 ohms. In simplex signaling applications, it introduces a series noninductive resistance of 10 ohms.

**2.16** The repeater introduces a series impedance at 20 Hertz which may vary from 150 to 250 ohms depending upon the gain and associated type of line. The series impedance will approach the lower value for lower gains. In general, for applications on cable circuits, the series impedance will affect the signaling range by an amount less than would otherwise be expected because of a favorable combination of the reactances of the line and of the repeater. For general design work, a 20-Hz ringing penalty of 150 ohms should be assumed for one series repeater and 250 ohms for two repeaters. No penalty need be assumed to the pulsing ranges on PC1, revertive, or dial pulsing trunks other than the dc resistance added by the repeater.

**2.17** The repeater is designed to withstand the maximum pulsing and ringing currents which occur in normal telephone usage. It will maintain stable repeater gain with dc loop currents up to 100 milliamperes.

#### Echo and Sidetone Effects

**2.18** If the repeater is adjusted to avoid singing or near-singing conditions, echo and sidetone effects will not generally be controlling factors in the design of any trunks other than toll connecting trunks and most special service lines. Echo considerations for toll connecting trunks are discussed in Section 852-305-100.

### 3. REPEATERS IN SERIES

#### A. General

**3.01** There are no transmission advantages in using two repeaters in series at one location rather than a single repeater. However, this condition may occur when two circuits equipped with terminal repeaters are switched together. In such cases, different gains will be obtained for the switched connections than for other connections, as discussed below. When E1 or E2 repeaters separated by line facilities are operated in series, the additional gains which may be obtained compared to the use of a single repeater depend on the loss and other characteristics of the intervening facilities, as discussed below.

#### B. Intermediate Repeaters

**3.02** In cases where two or more intermediate series repeaters are used on one circuit, computations to determine the maximum obtainable gain should be made as follows. Between any two repeaters, a 0-dB return loss is assumed at a point 0.55 of the total section loss away from each repeater. A return loss of 0 dB should also be assumed at each circuit terminal. The gain of each repeater is computed separately and the sum of these gains will give the maximum circuit gain obtainable. Where junctions of unlike facilities or other major irregularities exist, these points will generally be preferable repeater locations and result in higher total gains than those obtainable if the irregularity occurred between repeaters.

#### C. Terminal Repeaters on the Same Circuit

**3.03** The maximum obtainable gain for two terminal repeaters is computed in the same manner as for intermediate repeaters above. In general, there will be a small transmission advantage in the use of two terminal repeaters rather than a single repeater at a midpoint location.

#### D. Terminal Repeaters on Switched Circuits

**3.04** When two lines with terminal repeaters are switched together, the total gain obtained will be greater than the sum of individual gains. In such cases, the usable gain for each repeater will be determined by the return loss of its associated fixed line section as previously described. The gain which will then be obtained for switched connections may be determined by reading Fig. 1, using the return losses of the two fixed line sections associated with the terminal repeaters on the two switched lines. The curves are read in the same manner as if a single intermediate repeater were involved, as described earlier.

**3.05** If two terminal repeaters are operated with gains which differ from the usable gains which were assumed in 3.04, the resulting gain for the series combination may also be determined from Fig. 1. Assuming  $RL_B$  is 0 dB, locate a point corresponding to each repeater gain on the  $RL_A$  scale and read the resulting return loss values for  $RL_A$ . Use Fig. 1 in the normal manner to obtain the allowable gain for a single repeater with return losses equal to the two return loss values just determined. This gain will be that obtained when

the two terminal repeaters occur between circuits of approximately equal impedance.

**4. SPECIAL SERVICE LINE CONSIDERATIONS**

**A. General**

**4.01** In many special service line applications, it is possible to take advantage of specific terminating or equipment conditions to obtain a somewhat greater gain than that which would be obtainable in the case of switched circuits where the design usually requires stability in all terminal conditions. When idle circuit terminations can be used or when auxiliary equipment adjacent to the repeater is so arranged as to open the line in the idle condition (series repeater elements are basically open-circuit stable), the idle condition can be made less restrictive than the talking condition. In the case of idle circuit terminations or a fixed instrument termination, the idle circuit terminal return loss will be greater than zero and should be computed to determine the allowable idle circuit gain. When this terminal return loss is greater than zero, the maximum gain may be estimated in the case of loaded facilities from the curves in this section. For nonloaded facilities or for the case of the repeater between loaded and nonloaded facilities, reference should be made to Section 852-305-103. When the auxiliary equipment effectively opens the line at the repeater in the idle condition, the idle condition may be neglected as limiting the design and stability computations based on the talking condition, as discussed below.

**4.02** In either of the above cases, the talking condition of the line will usually be limiting and the attainable gain computed on that basis. A 6-dB return loss should be assumed at the point where the circuit is switched to trunks, loops, PBX stations, or connected to a telephone instrument. The terminal return loss and intermediate return losses, after correction for line loss, should be combined with the structural return loss on a power basis in the usual manner. However, a 26-dB return loss should be assumed on each side of the repeater to take care of variations in the network and other repeater characteristics. This should be added on a current-summation basis to the other return losses on each side of the repeater. These return losses should be added arithmetically and 10 dB deducted from the sum. One half of the remainder represents the estimated usable repeater gain under the talking condition. The 10

dB is included here to allow for variations from the assumed conditions.

**4.03** In general, the results obtained by the above estimates will indicate repeater gains of 1- to 5-dB greater for intermediate repeaters than would be indicated where the idle circuit condition is controlling and zero return losses apply at the terminals. In addition, should the special service line under consideration be connected to other repeated circuits, the requirements for operating repeaters in series should be met.

**4.04** In all instances where the above method of preselecting the usable repeater gain is followed, it will be desirable to make gain tests and adjustments in the network strapping when the circuit is lined up. This should include both the idle condition and the talking condition based on representative connections at the circuit terminals. Talking tests should also be made.

**4.05** Where idle circuit terminations are not provided or are impractical and higher gains are desirable, it would be advisable in all instances to make gain tests and to select the network strapping on the basis of the test results. It is probable that, in some cases, the return losses under the idle circuit condition may combine in a more favorable manner and higher gains may be obtained than indicated by the curves. Where this is the case, the measurements under the talking condition should be supplemented by talking tests on representative connections.

**B. Intermediate Signaling Equipment**

**4.06** In cases where intermediate signaling equipment is used, its presence in the line will have an effect not only on the maximum gain obtainable but also in some cases on the selection of the proper network strapping. As discussed above, if the intermediate equipment is so arranged as to open the line in the idle circuit condition, this usually eliminates the idle condition as controlling. In general, where such equipment is at the repeater location and the impedance presented by it under the idle condition is higher than the line impedance, the effect will be to decrease the relative importance of the idle condition and its effect on repeater gain. Where the signaling equipment is not near the repeater, particularly where loading facilities intervene, such equipment may increase or decrease the impedance as seen from the repeater. The

effect of this intermediate equipment on the proper network selection for the cases of loaded, nonloaded, and combination facilities is discussed in Section 852-305-103.

### C. Bridged Taps

**4.07** On special service lines where loop facilities are used adjacent to a repeater as a part of the fixed line, bridged taps are sometimes encountered. Where predetermined network strappings are to be used, the effect of such bridged taps on line loss should be neglected in using Fig. 3A or 3B to obtain the estimated usable repeater gain. In estimating the overall loss, however, the line loss caused by the bridged tap should be taken into account. For the situations where network adjustments are to be made during the circuit lineup, it can be assumed that approximately one-half of the added line loss due to the bridged

tap can be compensated for by gains higher than the estimated values from Fig. 3A and 3B.

### D. AC Operation of Repeaters

**4.08** In some special service applications, it may be desired to install these repeaters in locations where standard repeater power supply is not available and the number of repeaters proposed is too small to justify the provision of such a supply. In such cases, the repeaters may be operated on 110V ac power by means of a modified J68638A power supply unit. Each such unit will supply four series repeaters. Such use requires replacement of the 407A-type vacuum tube in the repeater with a type 396A tube to obtain 6.3-volt heater operation. It also requires strapping changes in both the power supply and the repeater. The details of these modifications are discussed in other sections of these practices.